

## Exercises for “Computer Science II” — SS 2003

No. 2

Due: May 17, 2003

---

### Number Systems

1. Convert the following numbers from one notation to another; intermediate steps are necessary. **(2 points)**

*Example:*  $555_{10} = 512 + 32 + 8 + 2 + 1 = 1000101011_2$

$$10110001011010_2 = \underline{\hspace{10cm}} \quad 16$$

$$1ED_{16} = \underline{\hspace{10cm}} \quad 8$$

$$11001.101_2 = \underline{\hspace{10cm}} \quad 10$$

$$10101.111_2 = \underline{\hspace{10cm}} \quad 10$$

$$555_8 = \underline{\hspace{10cm}} \quad 10$$

$$219_{10} = \underline{\hspace{10cm}} \quad 2$$

$$43.375_{10} = \underline{\hspace{10cm}} \quad 2$$

$$2^{26} = \underline{\hspace{10cm}} \quad 10$$

### Gate-Level Circuit Design

2. For each expression below, create a gate level implementation using only the specified types of gate. Use mixed logic notation (i.e., bubbled output go to bubbled inputs and non-bubbled outputs go to non-bubbled inputs). Do not assume you have the complements of the inputs. **(3 points)**

a)  $f = xy + yz$  using only NAND and OR gates

b)  $f = x + yz$  using only NOT, NAND and OR gates

c)  $f = (A + B)(C + D)$  using only NOR and AND gates

### Simplification of Boolean Expressions

3. For the truth table as shown in Fig. 1, give the minterm sum of product equation, and simplify the expression using Boolean algebra. **(2 points)**

x	y	z	F(x,y,z)
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

Figure 1: A truth table

### K-Maps

4. A desired logical function is specified in the Karnaugh map as shown in Fig. 2. Write the original expression and simplified sum of products (SOP) expression. Implement your SOP using AND, OR gates and inverters. (3 points)

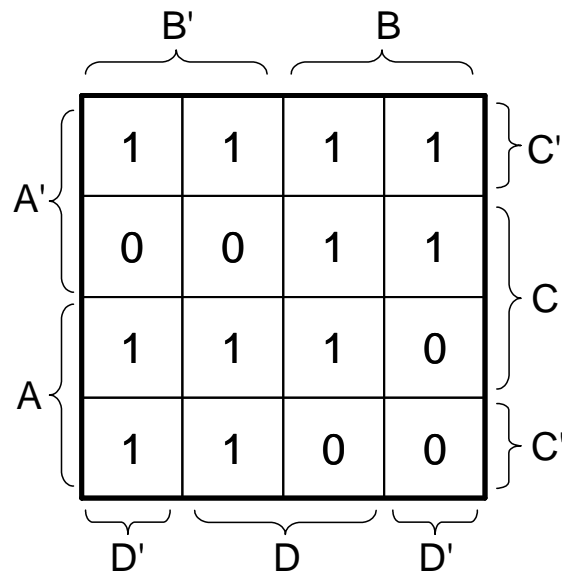


Figure 2: A Karnaugh map